


Name \rightarrow Priatham Pali

Roll no. \rightarrow 21H018


Sec no. \rightarrow 211112254

BEEE - 124

Q1)

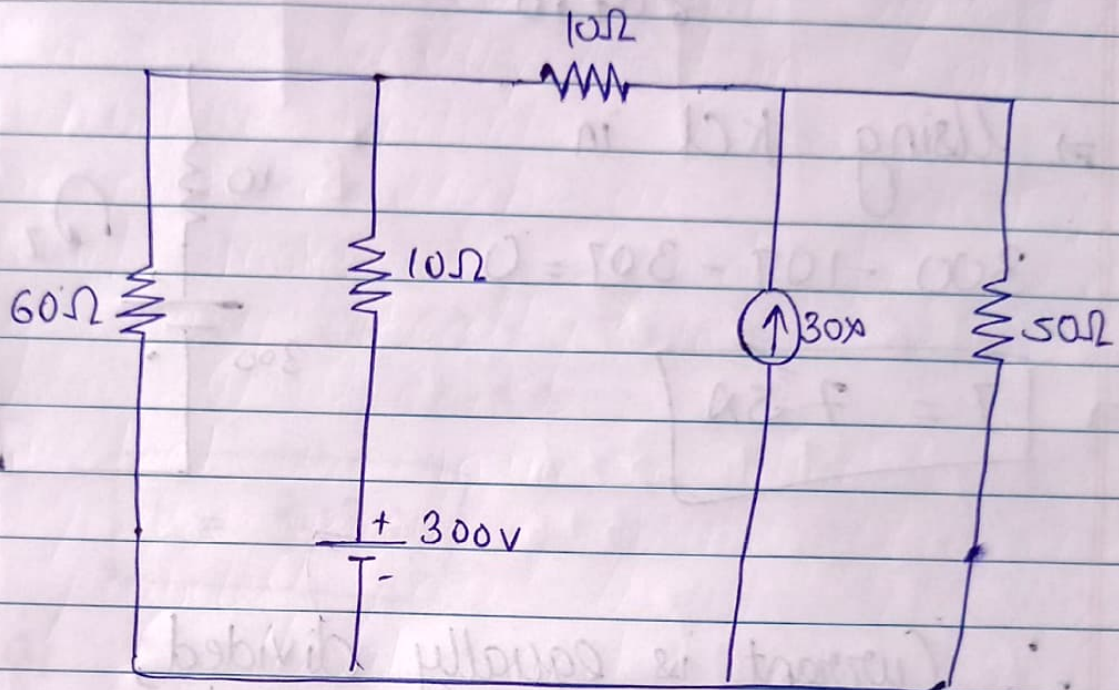

Q2) Considering 300V battery

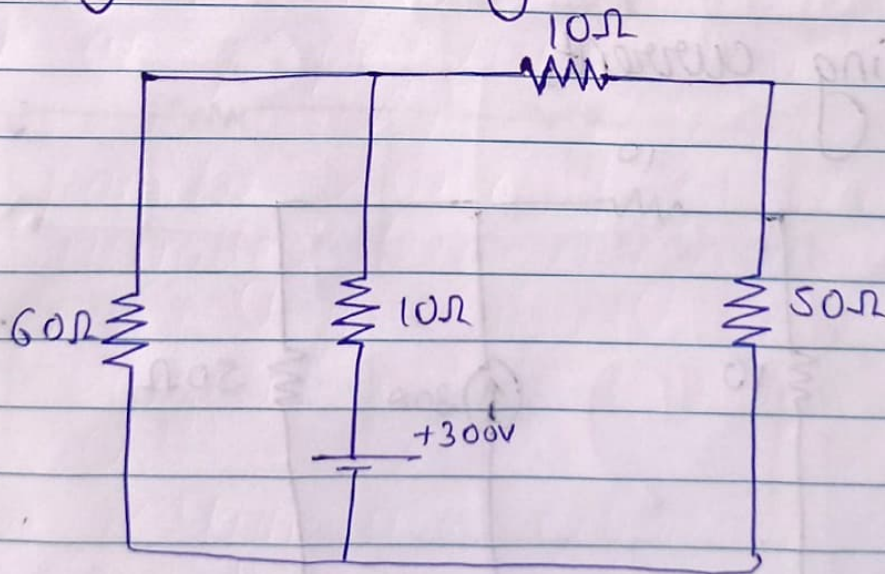

\because 10Ω & 50Ω are in parallel,

$$\Rightarrow R_{eq} = 10 + 50 \\ = 60\Omega.$$


Now 60Ω , ~~10Ω~~ , 60Ω are in parallel

$$\Rightarrow R_{eq} = \frac{60 \times 60}{60 + 60} = 30\Omega$$

\Rightarrow Using KCL in

$$300 - 10I - 30I = 0$$


$$\Rightarrow \boxed{I = 7.5A}$$

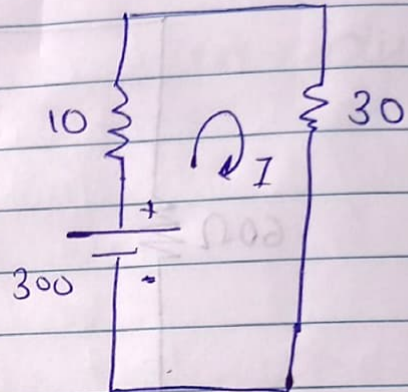

\therefore Current is equally divided,

$$\therefore \boxed{I \text{ in } 50\Omega \text{ resistance is } \frac{3.75}{2}A}$$

Considering current,

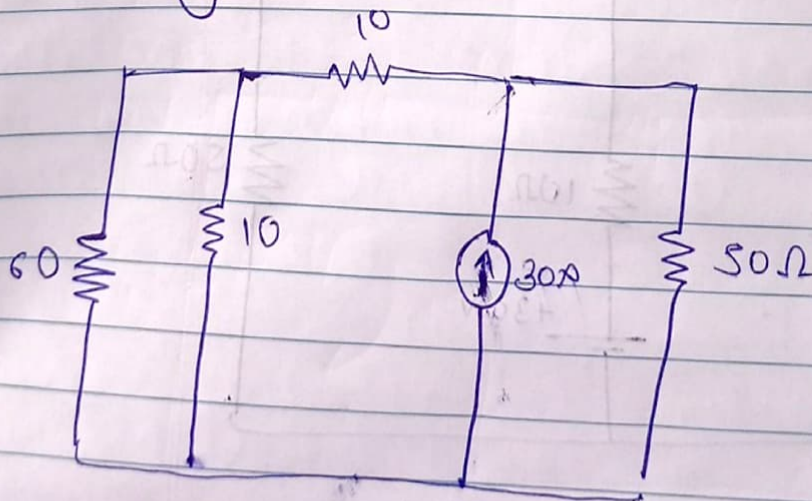

60 & 10 in parallel,

$$R = \frac{60 \times 10}{60 + 10} = \frac{600}{70} = \frac{60}{7}\Omega$$

10Ω & $\frac{60\Omega}{7}$ in series,

$$\Rightarrow R = \frac{70 + 60}{7} = \frac{130}{7} = 18.59\Omega$$

So I in 50Ω is

$$I = \frac{18.59 \times 30}{68.59}$$

$$I = 8.13A$$


\therefore Total current,

$$I = 7.5 + 8.13$$


$$I = 15.63A$$

$$I = 8.13 + 3.75 = 11.88A$$

(b)

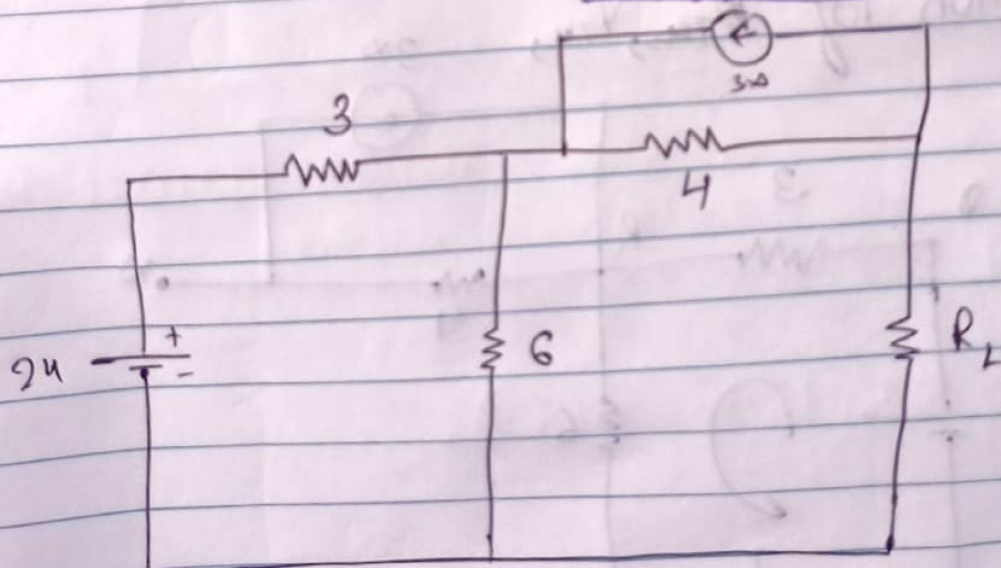

Calculation of R_{TH} ,

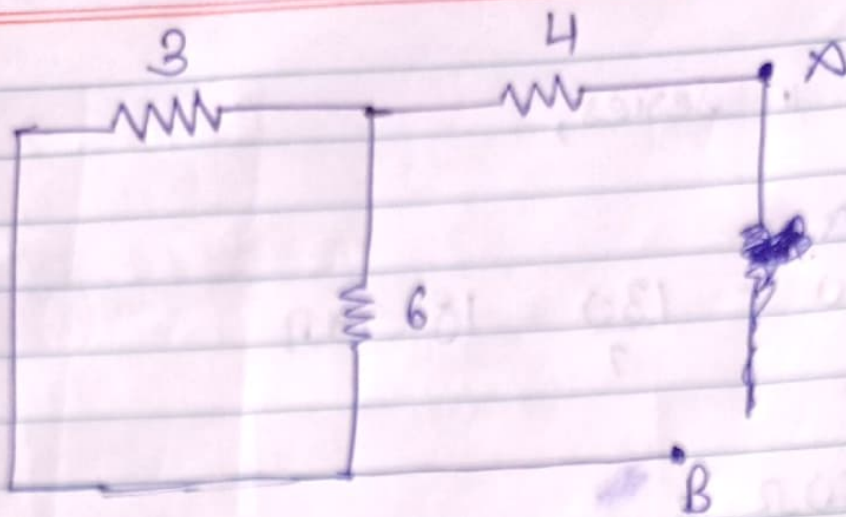


$$3 \parallel 6$$

$$R_{eq} = 4 + \frac{3 \times 6}{3 + 6}$$

$$R_{eq} = 6 \Omega$$

Calculation of R_{TH} , V_{TH} ,

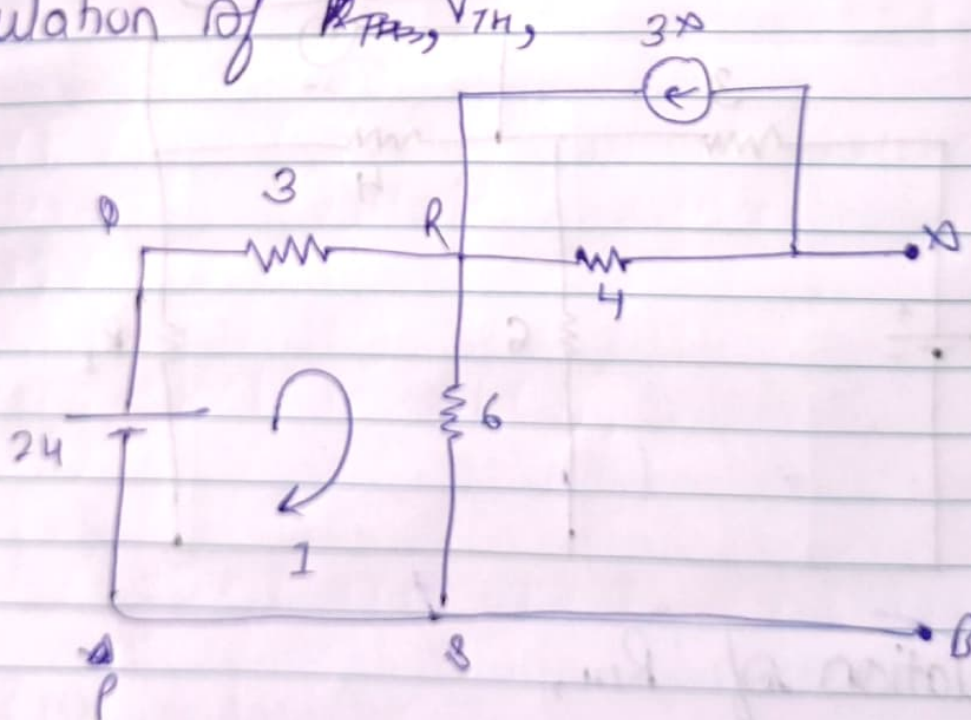

Apply KCL in node R,


$$+24 - 3I - 6I = 0$$

$$\Rightarrow I = \frac{24}{9} = 2.67 \text{ A}$$



$$\therefore V_A - 12 - 6 \times 2.67 = V_B$$

$$\Rightarrow \boxed{V_A - V_B = 4 \text{ V}}$$

Therefore thevenin equivalent is,

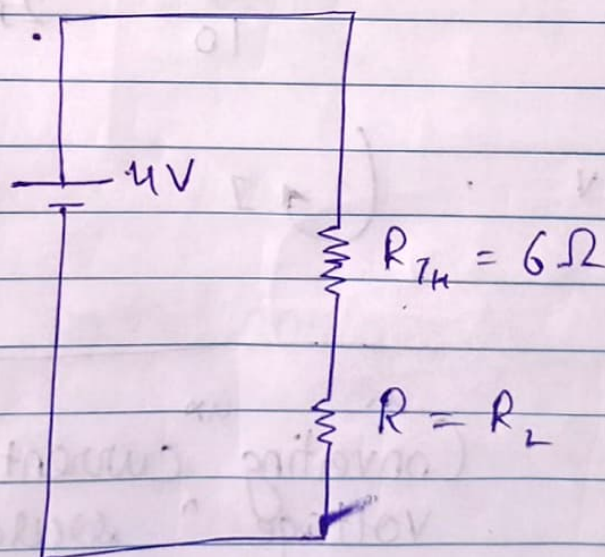

Q2 a)

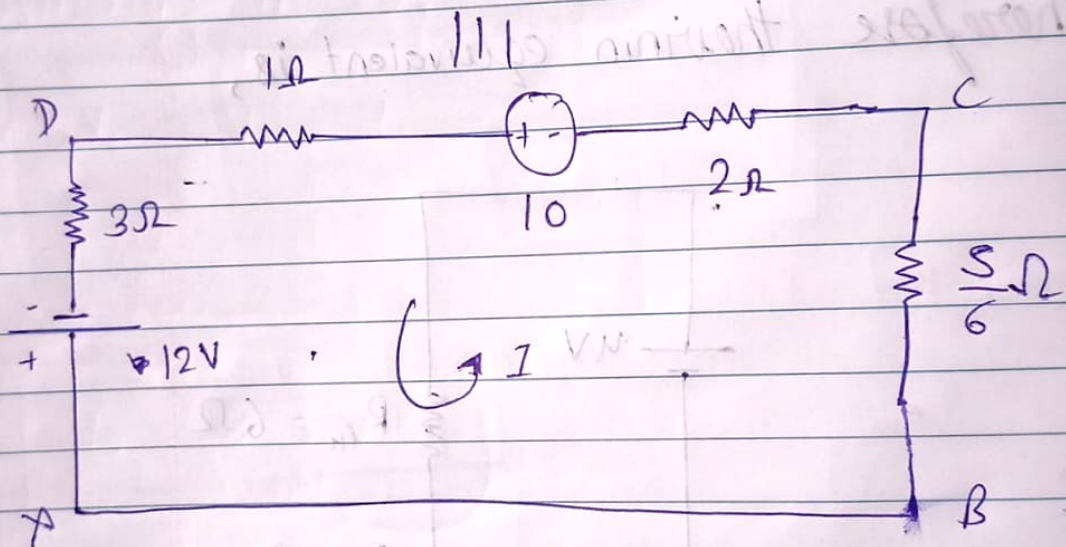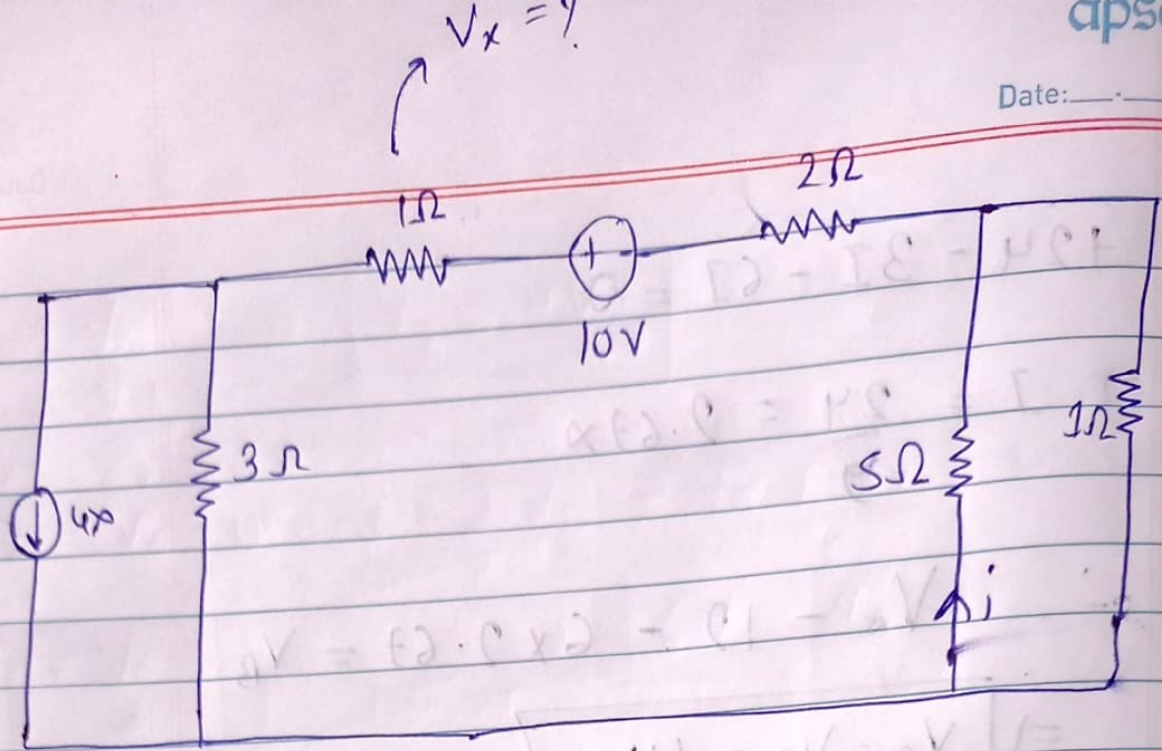

$$\begin{aligned} V &= IR \\ &= 4 \times 3 \\ &= 12V \end{aligned}$$

Converting current source into voltage source

Applying KCL in ABCD,

$$-\frac{5}{6} \times I - 2 \times I + 10 - 1 \times I - 3 \times I + 12 = 0$$


$$\Rightarrow \left(-\frac{5}{6} - 2 - 1 - 3 \right) I + 22 = 0$$

$$\Rightarrow I = \frac{22}{6.83} = 3.22A$$

$$\therefore V_x = IR$$

$$= 3.22 \times 1$$

$$\boxed{V_x = 3.22 \text{ V}}$$

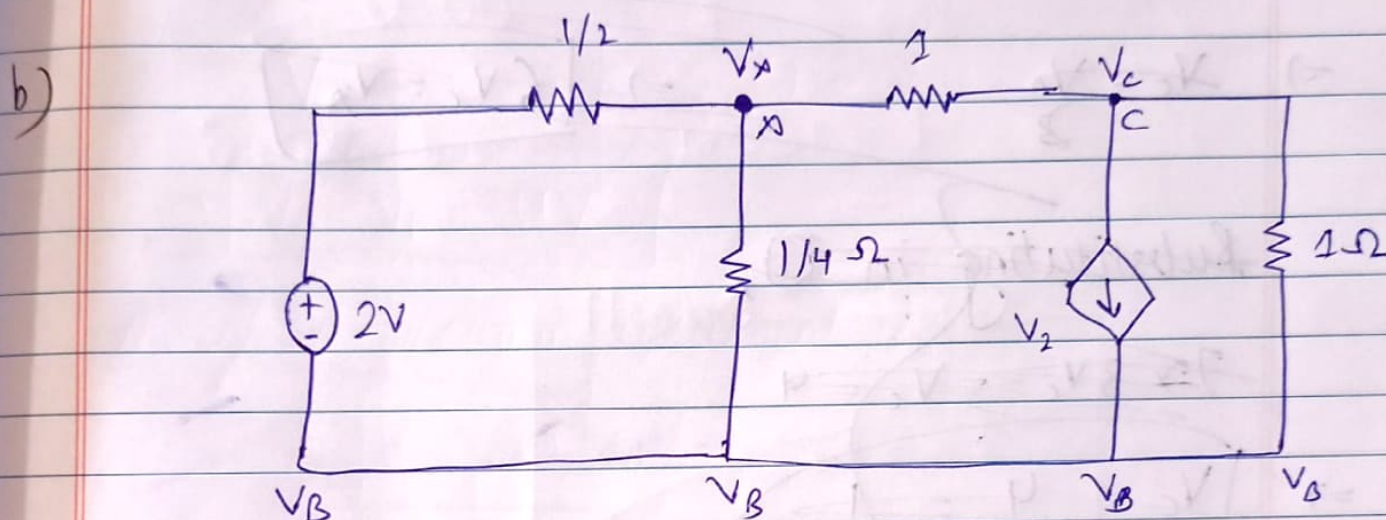

Sol) Let V_B be at 0

\therefore Applying nodal analysis at X,

$$\frac{V_x - 2 - 0}{1/2} + \frac{V_x - 0}{1/4} + \frac{V_x - V_c}{1} = 0$$

$$\Rightarrow 2V_x - 4 + 4V_x + V_x - V_c = 0$$

$$\Rightarrow \boxed{7V_x - V_c = 4} \quad \text{--- (1)}$$

Applying nodal analysis at C

$$\frac{V_c - V_x}{1} + V_2 + \frac{V_c - 0}{1} = 0$$

$$\Rightarrow 2V_c - V_x + V_2 = 0$$

$$V_2 = V_A$$

$$2V_C - V_A + V_2 = 0$$

$$\Rightarrow V_C = 0$$

$$\therefore V_A = \frac{4}{7}$$

$$\therefore V_1 = 2V$$

$$V_2 = V_A - V_B$$

$$V_2 = \frac{4}{7}V$$



$$V_3 = V_C - V_A$$

$$V_3 = 0$$

Q3 a) $Z_1 \Rightarrow$ For Z_1 , $\cos \phi = \frac{1}{2}$ Lagging

$$P = 100W$$

$$\phi = 48.6^\circ$$

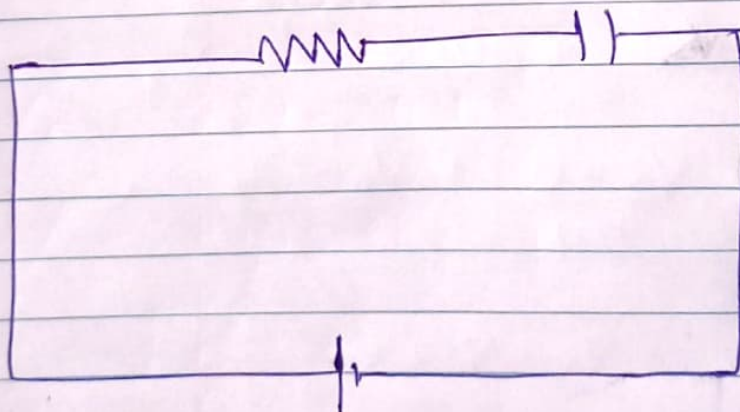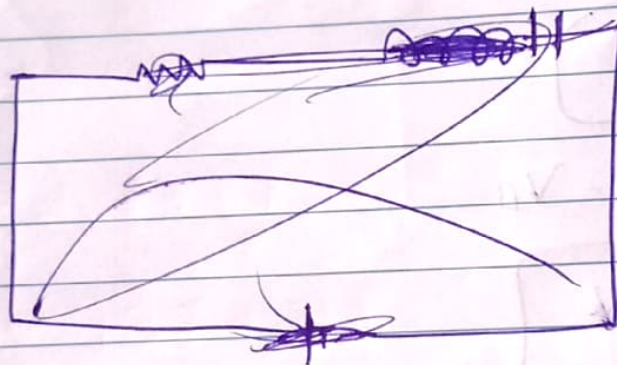

$$P = V I \cos \phi$$

$$\Rightarrow 100 = 230 \times I \times \frac{1}{2}$$

$$\Rightarrow I = \frac{20}{23} A$$

$$\therefore V = IZ$$

$$\Rightarrow Z = \frac{V}{I}$$

$$= \frac{230 \times 23}{20.75}$$

$$= 264.5$$

$$= 264.5$$

$$Z_1 = 132.25 \Omega$$

$$Z_1 = 264.5$$

$$Z_1 = 264.5 \angle -60^\circ$$

For Z_2 ,

$$\cos \phi = \frac{3}{5}, \quad P = 60$$

$$P = VI \cos \phi$$

$$\Rightarrow 60 = \frac{230}{5} \times I \times \frac{3}{5}$$

$$\Rightarrow I = \frac{10}{23}$$

$$Z_2 = \frac{230}{10} \times 23 =$$

$$Z_2 = 529 \Omega$$

$$Z_2 = 529 \angle 53.13^\circ$$

$$Z_{\text{eff}} = Z_1 + Z_2$$

$$= 264.5 \left(-\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) + 529 \left(\frac{3}{5} + j \frac{4}{5} \right)$$

$$= 449.65 + 200.31 - 203.47 + 194.14$$

$$Z = \sqrt{202.185 \cdot 1225 + 41265 \cdot 85}$$

$$= 489$$

$$P = \frac{V^2}{Z} = \frac{230 \times 230 \times 0.918}{489.76}$$

✱

$$R_{eq} = R_1 + R_2$$

$$= 132 + 318$$

$$= 450 \Omega$$

$$X_c = 229 - 414$$

$$= -195 \Omega$$

$$Z = \sqrt{R^2 + X^2}$$

$$= \sqrt{450 \times 450 + 195 \times 195}$$

$$Z = 490$$

(i) Total power absorbed

$$= I^2 R$$

$$= 0.472 \times 450$$

$$= 212.4$$

$$= 99 \text{ W}$$


$$\cos \phi = \frac{R}{Z} = \frac{450}{490} = 0.92 \text{ lead}$$

$$(ii) X_{\text{net}(C)} = X_{\text{net}(L)}$$

\therefore Reactance of required series pure inductive coil is 195Ω

$$Z = 195 \Omega$$

Q4) (b)

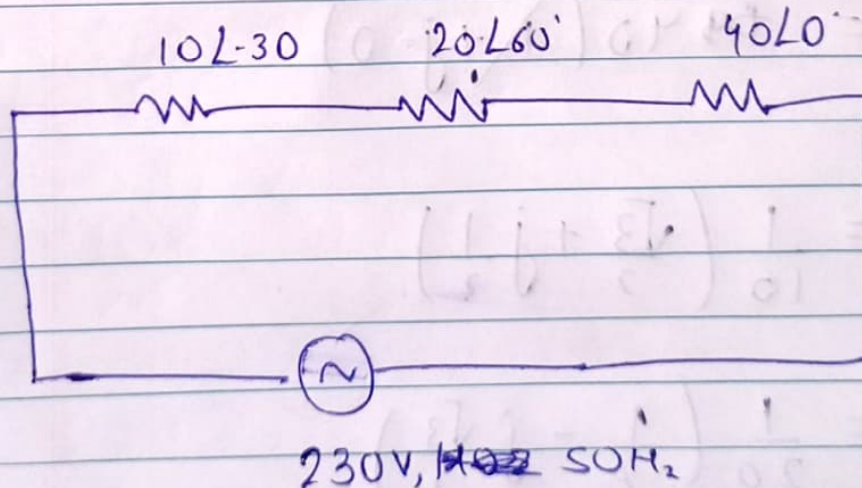

$$Z_1 = 10 \angle -30^\circ = 10(\cos -30^\circ + j \sin -30^\circ)$$

$$Z_1 = 10 \angle -30^\circ \quad Z_2 = 20 \angle 60^\circ$$

$$Y_1 = \frac{1}{10} \angle 30^\circ \quad Y_2 = \frac{1}{20} \angle -60^\circ$$

$$Z_3 = 40 \angle 0^\circ$$

$$Y_3 = \frac{1}{40} \angle 0^\circ$$

~~$$Z_1 = 10 \left(\frac{\sqrt{3}}{2} - j \frac{1}{2} \right)$$~~

~~$$Z_2 = 20 \left(\frac{1}{2} + j \frac{\sqrt{3}}{2} \right)$$~~

~~$$Z_3 = 40 (1 + j \cdot 0)$$~~

$$Y_1 = \frac{1}{10} \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right)$$

$$Y_2 = \frac{1}{20} \left(\frac{1}{2} - j \frac{\sqrt{3}}{2} \right)$$

$$Y_3 = \frac{1}{40} (1 + j \cdot 0)$$

$$\begin{aligned} Y_{\text{net}} &= 0.0865 + 0.025 + 0.025 + j(0.05 - 0.0433) \\ &= 0.1365 + j(0.0067) \end{aligned}$$

$$Y_{\text{net}} = 0.168 \text{ Simen}$$

$$\begin{aligned} \text{ii)} \quad Z_{\text{net}} &= (8.66 + 10 + 40) + j(-5 + 17.32) \\ &= 58.66 + 12.32j \end{aligned}$$

$$Z_{\text{net}} = 59.33$$

~~iii) Power Consumed~~

$$= \frac{V^2}{|Z|} \cos \phi$$

$$= \frac{230^2}{59.93} \times 0.9788$$

Power factor,

$$\cos \phi = \frac{58.66}{59.93}$$

$$= 0.9788 \text{ lead}$$

Power Consumed

$$= \frac{230 \times 230}{59.93} \times 0.9788$$

$$= 863.98 \text{ W}$$